

Proiect CID


Automat Bistabile

Vintila Nicolae-Daniel



Grupa: 2123

Proiect: 21-D-III

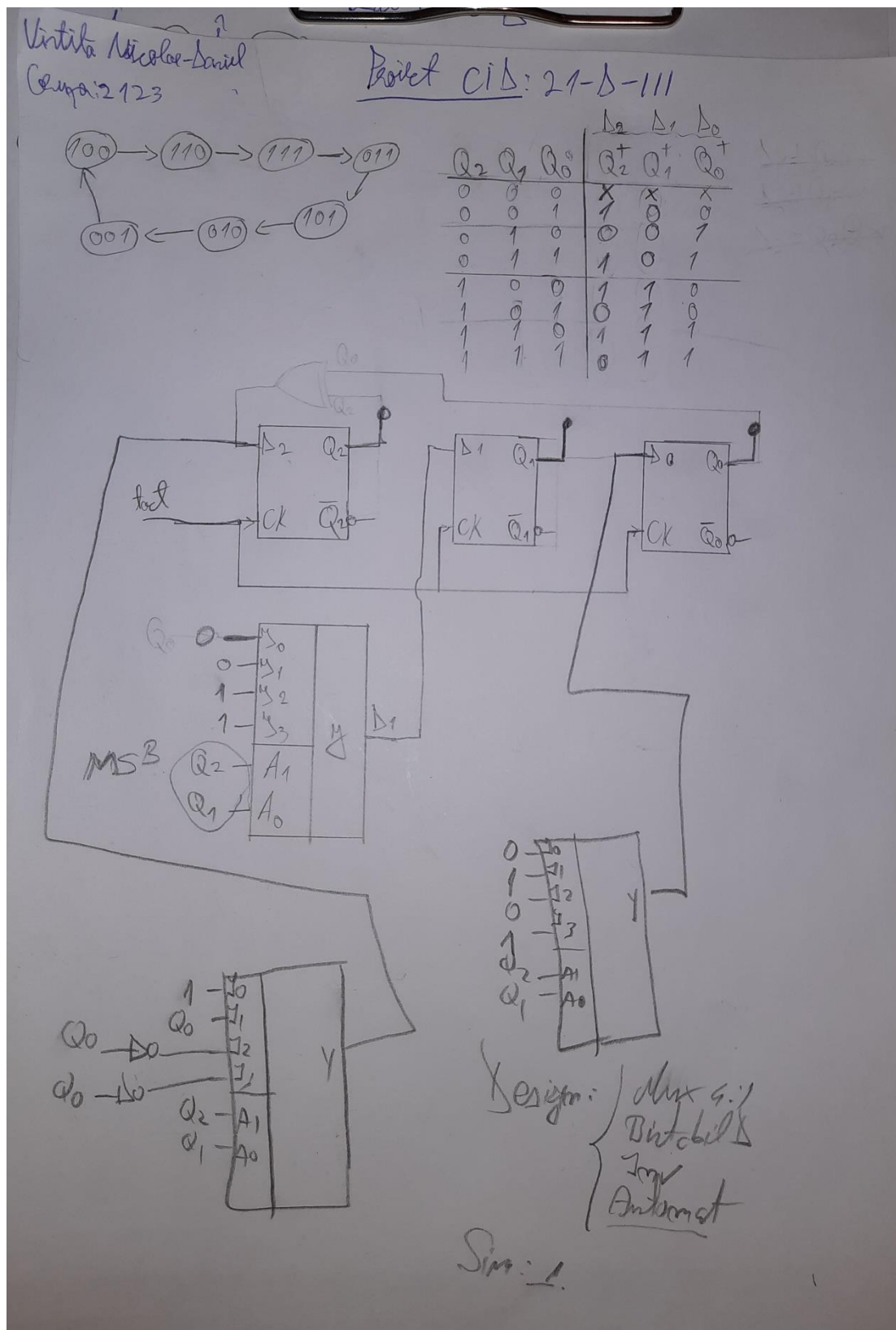1) Rezolvarea pe hartie a temei de proiect



 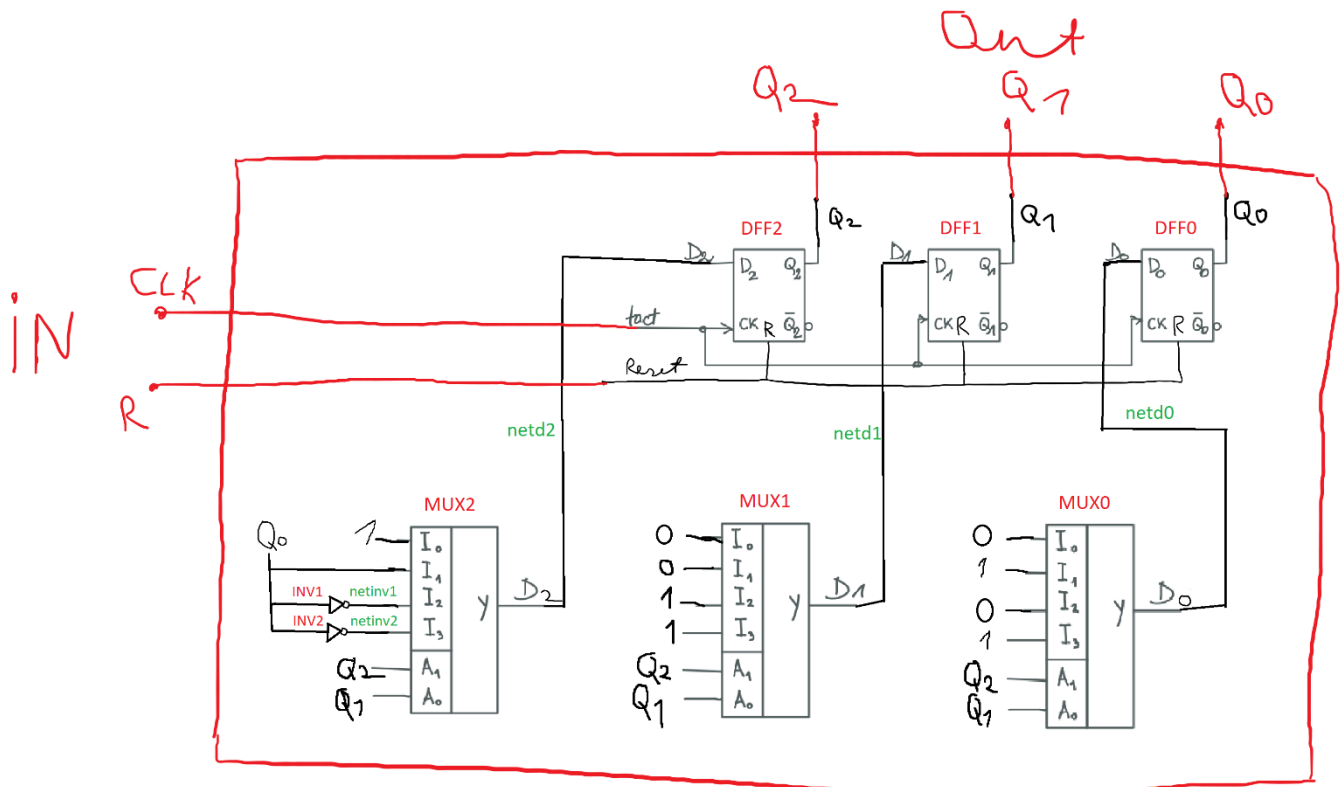2) Circuitul pentru implementarea in Vivado si tabelul de adevar



D.

r	clk	Action
1	x	Reset
0	$\overline{\text{L}}$	$Q^+ = D$
otherwise		Wait

III. MUX 4:1 și porți logice

3) Implementarea componentelor (Bistabilul D, MUX, Poarta inversor)

```
DFF.vhd x INV.vhd x MUX4.vhd x automat.vhd
D:/College Things/.An II/CID/Lab/Lab uri clasa/Automat_Vintila_N

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity DFF is
5     Port ( d : in STD_LOGIC;
6           clk : in STD_LOGIC;
7           r : in STD_LOGIC;
8           q : out STD_LOGIC;
9           qn : out STD_LOGIC);
10 end DFF;
11
12 architecture Behavioral of DFF is
13 begin
14
15 process(clk, r)
16 begin
17     if r='1' then
18         q <= '0';
19         qn <= '1';
20
21     elsif falling_edge(clk) then
22         q <= d;
23         qn <= not d;
24     end if;
25
26 end process;
27
28 end Behavioral;
```

```
DFF.vhd x INV.vhd x MUX4.vhd x automat.vhd
D:/College Things/.An II/CID/Lab/Lab uri clasa/Automat_Vintila_N

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity MUX4 is
5     Port ( i0 : in STD_LOGIC;
6           i1 : in STD_LOGIC;
7           i2 : in STD_LOGIC;
8           i3 : in STD_LOGIC;
9           a1 : in STD_LOGIC;
10          a0 : in STD_LOGIC;
11          y : out STD_LOGIC);
12 end MUX4;
13
14 architecture Behavioral of MUX4 is
15
16     signal a: std_logic_vector (1 downto 0);
17     begin
18
19         a <= a1 & a0;
20
21         with a select
22             y <= i0 when "00",
23                 i1 when "01",
24                 i2 when "10",
25                 i3 when "11",
26                 i0 when others;
27
28
29 end Behavioral;
```

```
DFF.vhd x INV.vhd x MUX4.vhd x aut
D:/College Things/.An II/CID/Lab/Lab uri clasa/Autor


1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity INV is
5     Port ( a : in STD_LOGIC;
6           y : out STD_LOGIC);
7 end INV;
8
9 architecture Behavioral of INV is
10
11 begin
12
13     y <= not a;
14
15 end Behavioral;
```

4) Implementarea sursei automatului

```
DFF.vhd x INV.vhd x MUX4.vhd x automat.vhd x Test_aut
D:/College Things/An II/CID/Lab/Lab uri clasa/Automat_Vintila_Nicolae-Daniel
Q [Save] [Undo] [Redo] [Cut] [Copy] [Paste] [Delete] [Comment] [Uncomment] [Find]
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity automat is
5     Port ( clk : in STD_LOGIC;
6           r : in STD_LOGIC;
7           q : out STD_LOGIC_VECTOR (2 downto 0));
8 end automat;
9
10 architecture Behavioral of automat is
11
12     component DFF is
13         Port ( d : in STD_LOGIC;
14               clk : in STD_LOGIC;
15               r : in STD_LOGIC;
16               q : out STD_LOGIC;
17               qn : out STD_LOGIC);
18     end component DFF;
19
20     component MUX4 is
21         Port ( i0 : in STD_LOGIC;
22               i1 : in STD_LOGIC;
23               i2 : in STD_LOGIC;
24               i3 : in STD_LOGIC;
25               a1 : in STD_LOGIC;
26               a0 : in STD_LOGIC;
27               y : out STD_LOGIC);
28     end component MUX4;
29
30     component INV is
31         Port ( a : in STD_LOGIC;
32               y : out STD_LOGIC);
33     end component INV;
34
35     signal netd0, netd1, netd2, netinv1, netinv2:std_logic;
36     signal qint:std_logic_vector(2 downto 0);
37
38     begin
39         q <= qint;
40
41         DFF0: DFF port map( clk => clk,
42                             r => r,
43                             d => netd0,
44                             q => qint(0));
```

```
DFF.vhd x INV.vhd x MUX4.vhd x automat
D:/College Things/An II/CID/Lab/Lab uri clasa/Automat_V
Q [Save] [Undo] [Redo] [Cut] [Copy] [Paste] [Delete] [Comment] [Uncomment] [Find]
44         q => qint(0));
45
46         DFF1: DFF port map ( clk => clk,
47                             r => r,
48                             d => netd1,
49                             q => qint(1));
50
51         DFF2: DFF port map ( clk => clk,
52                             r => r,
53                             d => netd2,
54                             q => qint(2));
55
56         MUX0: MUX4 port map (i0 => '0',
57                             i1 => '1',
58                             i2 => '0',
59                             i3 => '1',
60                             a1 => qint(2),
61                             a0 => qint(1),
62                             y => netd0);
63
64         MUX1: MUX4 port map (i0 => '0',
65                             i1 => '0',
66                             i2 => '1',
67                             i3 => '1',
68                             a1 => qint(2),
69                             a0 => qint(1),
70                             y => netd1);
71
72         MUX2: MUX4 port map (i0 => '1',
73                             i1 => qint(0),
74                             i2 => netinv1,
75                             i3 => netinv2,
76                             a1 => qint(2),
77                             a0 => qint(1),
78                             y => netd2);
79
80         INV1: INV port map (a => qint(0),
81                             y => netinv1);
82
83         INV2: INV port map (a => qint(0),
84                             y => netinv2);
85
86     end Behavioral;
87
```

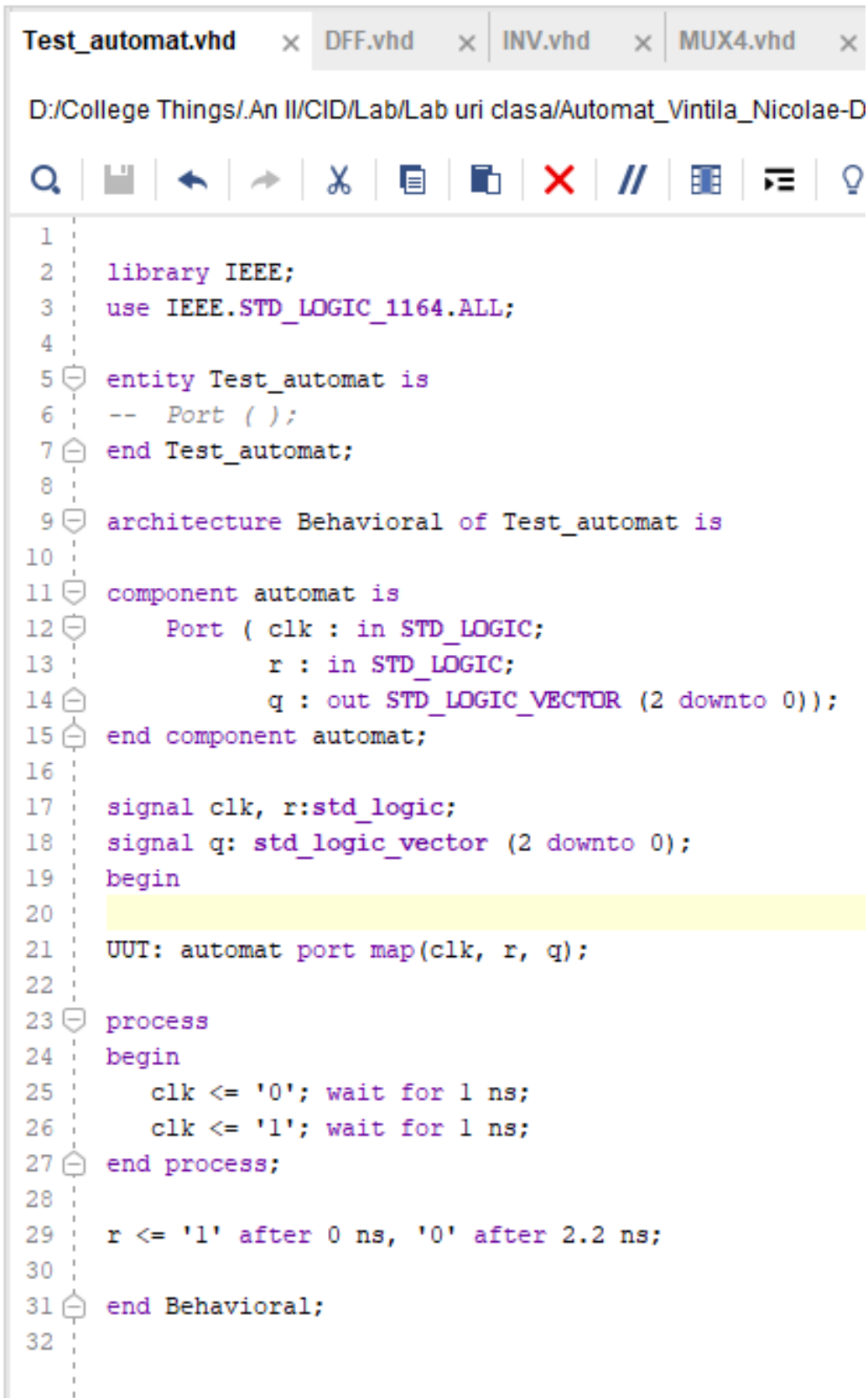5) Implementarea sursei de simulare a automatului



```
Test_automat.vhd x DFF.vhd x INV.vhd x MUX4.vhd x
D:/College Things/An II/CID/Lab/Lab uri clasa/Automat_Vintila_Nicolae-D

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4
5 entity Test_automat is
6 -- Port ( );
7 end Test_automat;
8
9 architecture Behavioral of Test_automat is
10
11 component automat is
12 Port ( clk : in STD_LOGIC;
13       r : in STD_LOGIC;
14       q : out STD_LOGIC_VECTOR (2 downto 0));
15 end component automat;
16
17 signal clk, r:std_logic;
18 signal q: std_logic_vector (2 downto 0);
19 begin
20
21 UUT: automat port map(clk, r, q);
22
23 process
24 begin
25     clk <= '0'; wait for 1 ns;
26     clk <= '1'; wait for 1 ns;
27 end process;
28
29 r <= '1' after 0 ns, '0' after 2.2 ns;
30
31 end Behavioral;
32
```

6) Implementarea sursei de simulare a bistabilului si portii inversoare

Test_BIST_D.vhd * x Test_MUX4.vhd x Test_inv.vhd

D:/College Things/An II/CID/Lab/Lab uri clasa/Automat_Vintila_Nic

Q

📁

↶

↷

✂

📄

📄

✖

//

🔍

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity Test_BIST_D is
5   -- Port ( );
6 end Test_BIST_D;
7
8 architecture Behavioral of Test_BIST_D is
9
10 component DFF is
11   Port ( d : in STD_LOGIC;
12         clk : in STD_LOGIC;
13         r : in STD_LOGIC;
14         q : out STD_LOGIC;
15         qn : out STD_LOGIC);
16 end component DFF;
17
18 signal d, clk, r, q, qn:std_logic;
19
20 begin
21
22 UUT: DFF port map(d, clk, r, q, qn);
23
24 process
25 begin
26   clk <= '0'; wait for 1 ns;
27   clk <= '1'; wait for 1 ns;
28 end process;
29
30 process
31 begin
32   d <= '0'; wait for 3.8 ns;
33   d <= '1'; wait for 3.8 ns;
34 end process;
35
36 r <= '1' after 0 ns, '0' after 2.3 ns;
37
38 end Behavioral;
```

Test_BIST_D.vhd x Test_inv.vhd x Test_MUX4

D:/College Things/An II/CID/Lab/Lab uri clasa/Automat_Vi

Q

📁

↶

↷

✂

📄

📄

✖

//

🔍


```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity Test_inv is
5   -- Port ( );
6 end Test_inv;
7
8 architecture Behavioral of Test_inv is
9
10 component INV is
11   Port ( a : in STD_LOGIC;
12         y : out STD_LOGIC);
13 end component INV;
14
15 signal a, y:std_logic;
16
17 begin
18
19 UT: INV port map (a, y);
20
21 process
22 begin
23   a <= '0'; wait for 2 ns;
24   a <= '1'; wait for 2 ns;
25 end process;
26
27 end Behavioral;
```

7) Implementarea sursei de simulare a multiplexorului 4:1


```
Test_BIST_D.vhd x Test_MUX4.vhd x Test_inv.vhd
D:/College Things/An II/CID/Lab/Lab uri clasa/Automat_Vintila_N

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity Test_MUX4 is
5  -- Port ( );
6  end Test_MUX4;
7
8  architecture Behavioral of Test_MUX4 is
9
10 component MUX4 is
11 Port ( i0 : in STD_LOGIC;
12        i1 : in STD_LOGIC;
13        i2 : in STD_LOGIC;
14        i3 : in STD_LOGIC;
15        a1 : in STD_LOGIC;
16        a0 : in STD_LOGIC;
17        y : out STD_LOGIC);
18 end component MUX4;
19
20 signal i0, i1, i2, i3, a1, a0, y: std_logic;
21
22 begin
23 UT: MUX4 port map(i0, i1, i2, i3, a1, a0, y);
24
25 process
26 begin
27 a0 <= '0'; wait for 2 ns;
28 a0 <= '1'; wait for 2 ns;
29 end process;
30
31 process
32 begin
33 a1 <= '0'; wait for 3 ns;
34 a1 <= '1'; wait for 3 ns;
35 end process;
36
37 process
38 begin
39 i0 <= '0'; wait for 4 ns;
40 i0 <= '1'; wait for 4 ns;
41 end process;
42
43 process
44 begin
45 i1 <= '0'; wait for 5 ns;
46 i1 <= '1'; wait for 5 ns;
47 end process;
48
49 process
50 begin
51 i2 <= '0'; wait for 6 ns;
52 i2 <= '1'; wait for 6 ns;
53 end process;
54
55 process
56 begin
57 i3 <= '0'; wait for 7 ns;
58 i3 <= '1'; wait for 7 ns;
59 end process;
60
61 end Behavioral;
62
```



8) Simulare propriu-zisa a automatului

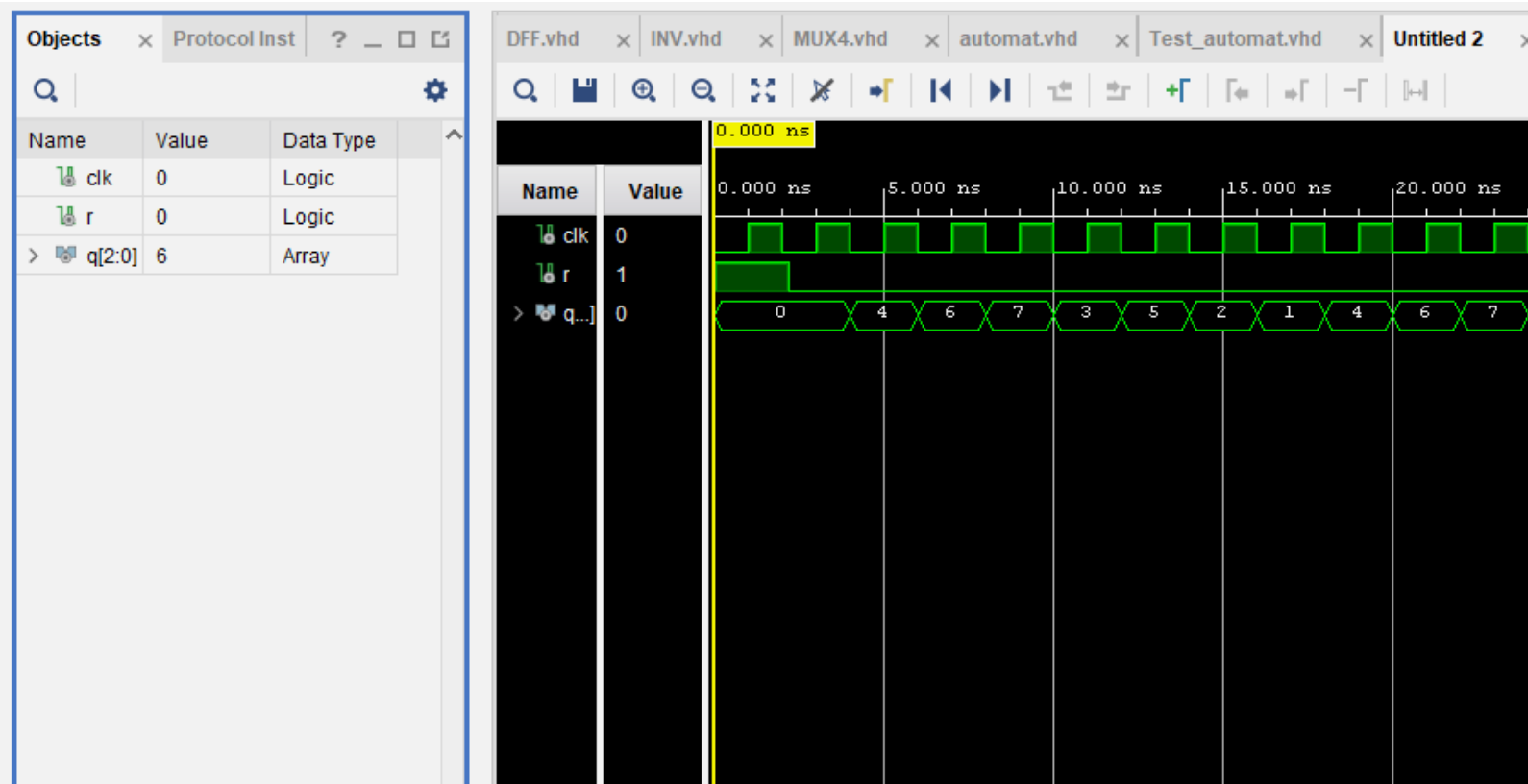


9) Simularea Bistabilului D

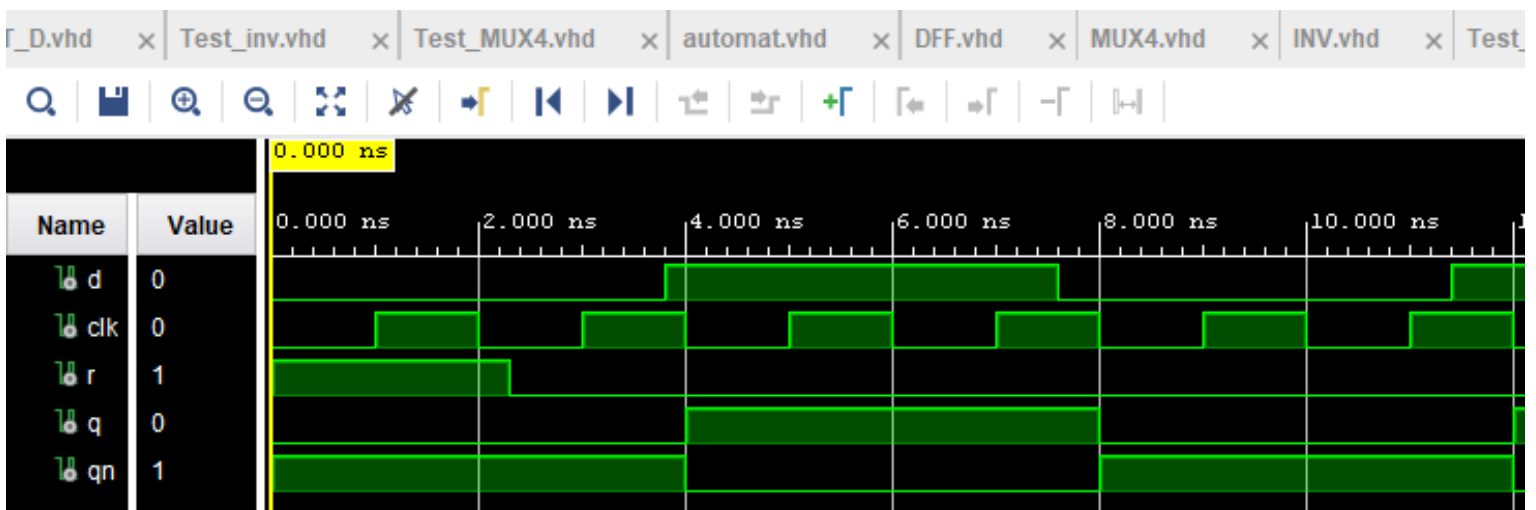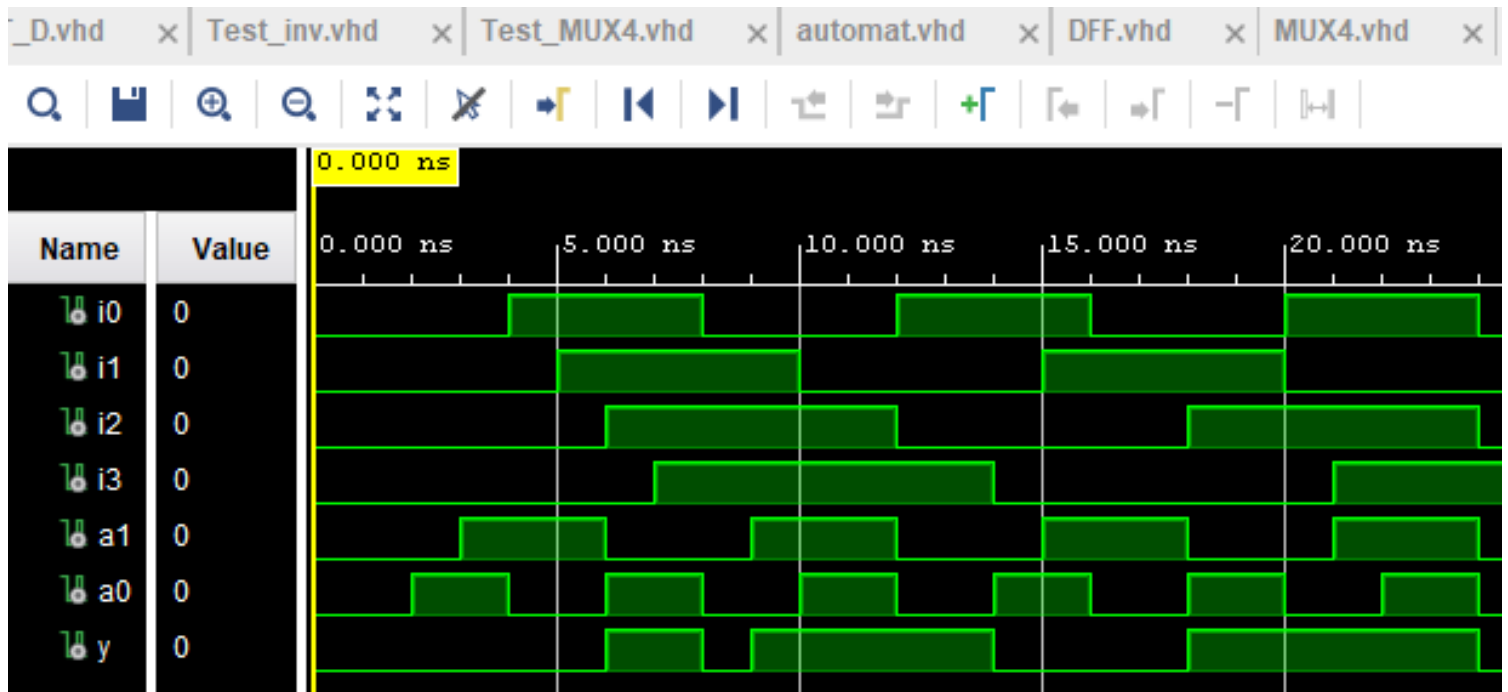

10) Simularea multiplexorului 4:1



11) Simularea portii inversoare

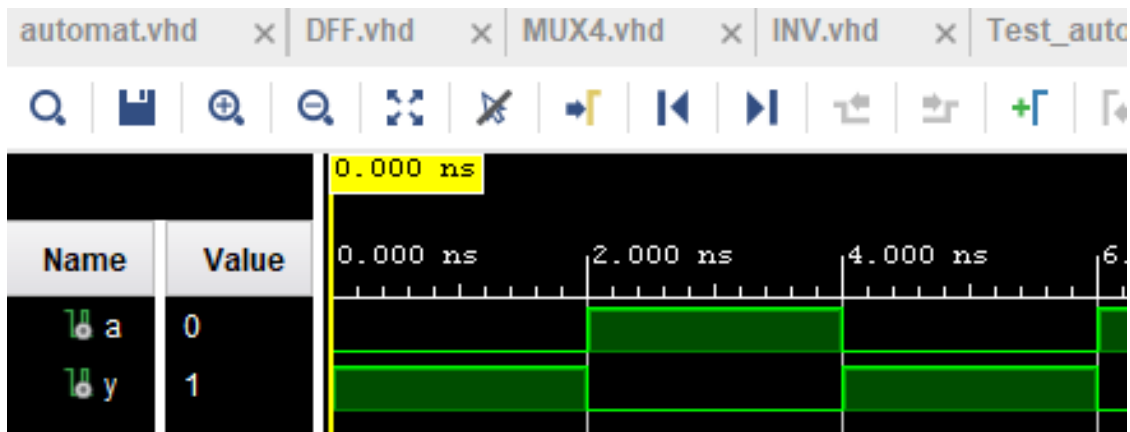

Multumesc de atentie!

Vintila Nicolae-Daniel

Grupa: 2123

Proiect: 21-D-III